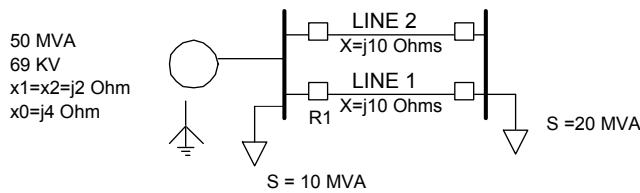


Do the following for the system below:



A. Sketch per unit circuits for the system in the sequence domain. Use $V_{b-ll} = 69 \text{ kV}$ and $S_B^{3\phi} = 50 \text{ MVA}$. Assume the lines have equal impedance in positive and negative sequence and three times the reactance in the zero sequence.

Define units: $\text{MVA} := 1000 \text{ kW}$ $\text{MW} := \text{MVA}$ $\text{MVA}_r := \text{MVA}$

Define transformation

$$a := 1 \cdot e^{j \cdot \frac{2 \cdot \pi}{3}}$$

$$A1 := \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix}$$

$$V_b := 69 \text{ kV} \quad S_b := 50 \text{ MVA} \quad V_{bln} := \frac{V_b}{\sqrt{3}}$$

$$Z_b := \frac{V_b^2}{S_b} \quad Z_b = 95.22 \Omega \quad I_b := \frac{S_b}{3 \cdot V_{bln}}$$

System impedances in ohms:

$$\begin{aligned} Z_{src0} &:= j \cdot 4 \text{ ohm} & Z_{line1_0} &:= j \cdot 30 \text{ ohm} & Z_{line2_0} &:= j \cdot 30 \text{ ohm} \\ Z_{src1} &:= j \cdot 2 \text{ ohm} & Z_{line1_1} &:= j \cdot 10 \text{ ohm} & Z_{line2_1} &:= j \cdot 10 \text{ ohm} \\ Z_{src2} &:= Z_{src1} & Z_{line1_2} &:= j \cdot 10 \text{ ohm} & Z_{line2_2} &:= j \cdot 10 \text{ ohm} \end{aligned}$$

System Impedances in per unit

$$\begin{aligned} Z_{src0pu} &:= \frac{Z_{src0}}{Z_b} & Z_{line1_0pu} &:= \frac{Z_{line1_0}}{Z_b} & Z_{line2_0pu} &:= \frac{Z_{line2_0}}{Z_b} \\ Z_{src0pu} &= 0.042i & Z_{line1_0pu} &= 0.3151i & Z_{line2_0pu} &= 0.3151i \\ Z_{src1pu} &:= \frac{Z_{src1}}{Z_b} & Z_{line1_1pu} &:= \frac{Z_{line1_1}}{Z_b} & Z_{line2_1pu} &:= \frac{Z_{line2_1}}{Z_b} \\ Z_{src1pu} &= 0.021i & Z_{line1_1pu} &= 0.105i & Z_{line2_1pu} &= 0.105i \end{aligned}$$

$$Z_{src2pu} := Z_{src1pu} \quad Z_{line1_2pu} := Z_{line1_1pu} \quad Z_{line2_2pu} := Z_{line2_1pu}$$

Loads (model as series impedance)

$$S_{load1} := 10MVA$$

$$S_{load2} := 20MVA$$

$$p_{load1} := 0.8$$

$$p_{load2} := 0.8$$

$$magZ_{ld1} := \frac{V_b^2}{S_{load1}}$$

$$magZ_{ld2} := \frac{V_b^2}{S_{load2}}$$

$$\theta_1 := \arccos(0.8) \quad \theta_1 = 36.8699 \text{ deg}$$

$$\theta_2 := \theta_1 = 36.8699 \text{ deg}$$

$$Z_{load1} := magZ_{ld1} \cdot e^{j \cdot \theta_1}$$

$$Z_{load2} := magZ_{ld2} \cdot e^{j \cdot \theta_2}$$

$$R_{load1} := \operatorname{Re}(Z_{load1}) \quad R_{load1} = 380.88 \Omega$$

$$R_{load2} := \operatorname{Re}(Z_{load2}) \quad R_{load2} = 190.44 \Omega$$

$$X_{load1} := \operatorname{Im}(Z_{load1}) \quad X_{load1} = 285.66 \Omega$$

$$X_{load2} := \operatorname{Im}(Z_{load2}) \quad X_{load2} = 142.83 \Omega$$

Model as being the same in positive and negative sequence, and open (ungrounded) in zero sequence)

$$R_{ld1_pu_pos} := \frac{R_{load1}}{Z_b} \quad R_{ld1_pu_pos} = 4$$

$$R_{ld2_pu_pos} := \frac{R_{load2}}{Z_b} \quad R_{ld2_pu_pos} = 2$$

$$R_{ld1_pu_neg} := R_{ld1_pu_pos}$$

$$R_{ld2_pu_neg} := R_{ld2_pu_pos}$$

$$X_{ld1_pu_pos} := \frac{X_{load1}}{Z_b} \quad X_{ld1_pu_pos} = 3$$



$$X_{ld2_pu_pos} := \frac{X_{load2}}{Z_b} \quad X_{ld2_pu_pos} = 1.5$$

$$X_{ld1_pu_neg} := X_{ld1_pu_pos}$$


$$X_{ld2_pu_neg} := X_{ld2_pu_pos}$$

Positive sequence equivalent:

Negative sequence equivalent:

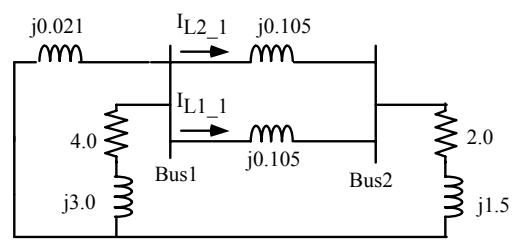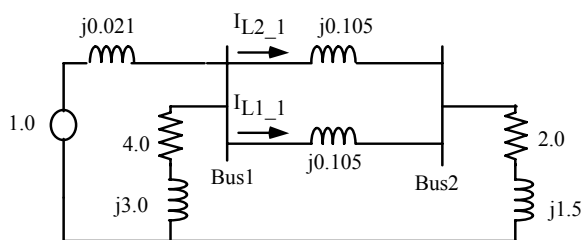

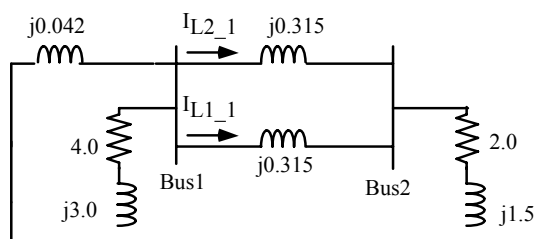Zero Sequence Equivalent:
note that the loads are open.



B. Compute the voltages and currents seen at point R1 for the following faults located at 10% and 90% of the way down line 1 from the source end: SLG, 3 ϕ , LL, DLG, and Phase "a" open. Also sketch phasor diagrams. Set the fault impedances at zero.

First calculate sequence equivalent impedances to the fault (with loads neglected)

Positive Sequence:

$$ZL1_left_pos := 0.1 \cdot Zline1_1pu \quad ZL1_left_pos = 0.0105i$$

$$ZL1_right_pos := 0.9 \cdot Zline1_1pu \quad ZL1_right_pos = 0.0945i$$

$$Z_{th1} := Z_{src1pu} + \left[\frac{1}{ZL1_left_pos} + \left(\frac{1}{Zline2_1pu + ZL1_right_pos} \right) \right]^{-1} \quad Z_{th1} = 0.031i$$

Negative Sequence:

$$ZL1_left_neg := 0.1 \cdot Zline1_2pu \quad ZL1_left_neg = 0.0105i$$

$$ZL1_right_neg := 0.9 \cdot Zline1_2pu \quad ZL1_right_neg = 0.0945i$$

$$Z_{th2} := Z_{src2pu} + \left[\frac{1}{ZL1_left_neg} + \left(\frac{1}{Zline2_2pu + ZL1_right_neg} \right) \right]^{-1} \quad Z_{th2} = 0.031i$$

Zero Sequence:

$$ZL1_left_0 := 0.1 \cdot Zline1_0pu \quad ZL1_left_0 = 0.0315i$$



$$ZL1_right_0 := 0.9 \cdot Zline1_0pu \quad ZL1_right_0 = 0.2836i$$

$$Z_{th0} := Z_{src0pu} + \left[\frac{1}{ZL1_left_0} + \left(\frac{1}{Zline2_0pu + ZL1_right_0} \right) \right]^{-1} \quad Z_{th0} = 0.0719i$$

Now repeat the calculations with the loads included (the zero sequence won't change) to see how much impact the loads will have on the calculations.

Positive sequence:

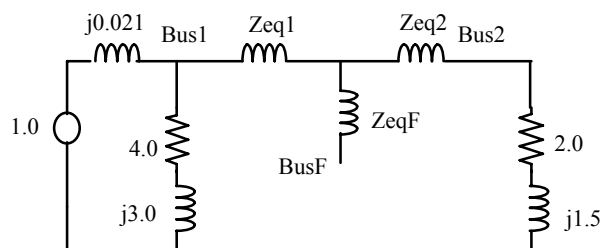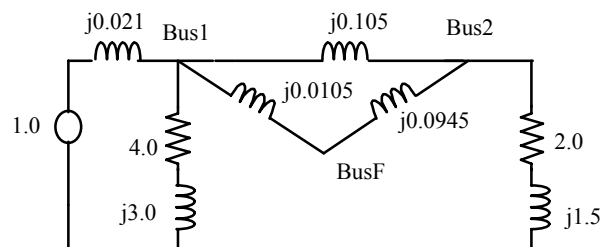The fault basically creates a Delta in the middle of the system (the corners of the delta are the buses at the end of the lines and the fault point). Convert this to a Y to make it easier to add in the loads



$$Z_{eq1_1} := \frac{Z_{line2_1pu} \cdot 0.1 \cdot Z_{line1_1pu}}{Z_{line2_1pu} + 0.1 \cdot Z_{line1_1pu} + 0.9 \cdot Z_{line1_1pu}} \quad Z_{eq1_1} = 5.251i \times 10^{-3}$$

$$Z_{eq2_1} := \frac{Z_{line2_1pu} \cdot 0.9 \cdot Z_{line1_1pu}}{Z_{line2_1pu} + 0.1 \cdot Z_{line1_1pu} + 0.9 \cdot Z_{line1_1pu}} \quad Z_{eq2_1} = 0.0473i$$

$$Z_{eqf_1} := \frac{0.1 Z_{line1_1pu} \cdot 0.9 \cdot Z_{line1_1pu}}{Z_{line2_1pu} + 0.1 \cdot Z_{line1_1pu} + 0.9 \cdot Z_{line1_1pu}} \quad Z_{eqf_1} = 4.7259i \times 10^{-3}$$

If there is no fault, then the equivalent for the line is

$$Z_{eq1_1} + Z_{eq2_1} = 0.0525i \quad \text{hich is} \quad \frac{Z_{line1_1pu}}{2} = 0.0525i \quad \text{as expected.}$$

So the positive sequence impedance looking in from BusF is made up Z_{eqf_1} plus the parallel impedances of the other paths:

$$Z_{left_1} := Z_{eq1_1} + \left(\frac{1}{Z_{src1pu}} + \frac{1}{R_{ld1_pu_pos} + j \cdot X_{ld1_pu_pos}} \right)^{-1} \quad Z_{left_1} = 7.0232 \times 10^{-5} + 0.0262i$$

$$Z_{right_1} := Z_{eq2_1} + R_{ld2_pu_pos} + j \cdot X_{ld2_pu_pos}$$

$$Z_{equiv1_act} := Z_{eqf_1} + \left(\frac{1}{Z_{left_1}} + \frac{1}{Z_{right_1}} \right)^{-1} \quad Z_{equiv1_act} = 2.8137 \times 10^{-4} + 0.0308i$$

$$\text{and earlier we found} \quad Z_{thv1} = 0.031i$$


So there is a small difference:

$$\text{Error} := \frac{|Z_{equiv1_act}| - |Z_{thv1}|}{|Z_{equiv1_act}|} \quad \text{Error} = -0.7142\% \quad \text{This is a smaller error than there is in the model data.}$$

The negative sequence impedances will be the same.

So for all calculations expect the phase A open, the loads will be neglected

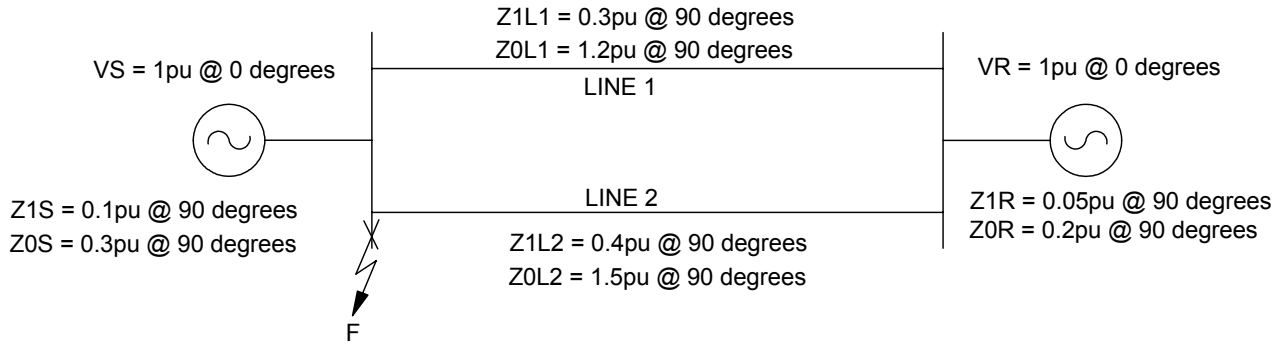4. For the following system with all quantities shown in per unit:
 - a. Develop the each of the sequence networks for a fault at location F.
 - b. Develop the sequence network connections for single-phase to ground, phase-phase to ground, phase-phase, and three-phase faults.
 - c. Determine the positive-, negative-, and zero-sequence currents and voltages at location F for a single-phase to ground fault.




$$a := 1 \cdot e^{j \cdot 120 \text{deg}}$$

$$A_{012} := \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix}$$

$$\text{pu} := 1$$

$$\text{ORIGIN} := 1$$

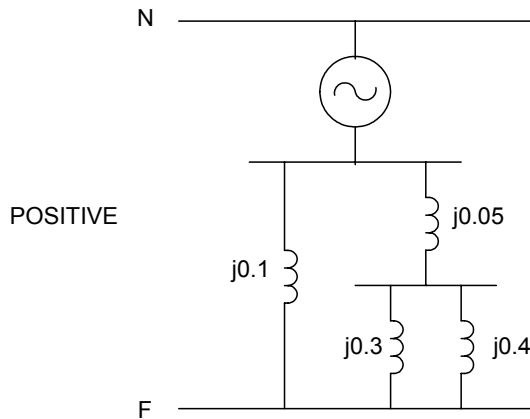Solution for 4a: Develop the each of the sequence networks for a fault at location F.




$$Z_{1S} := j \cdot 0.1 \text{pu} \quad Z_{1R} := j \cdot 0.05 \text{pu}$$

$$Z_{1L1} := j \cdot 0.3 \quad Z_{1L2} := j \cdot 0.4$$

$$Z_{1\text{LineEq}} := \left(\frac{1}{Z_{1L1}} + \frac{1}{Z_{1L2}} \right)^{-1}$$

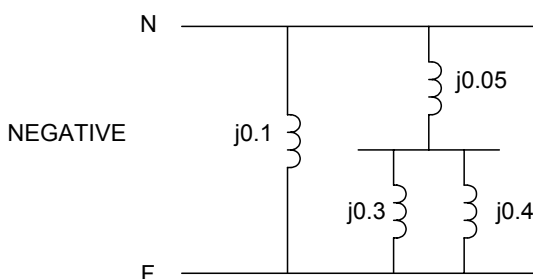
$$Z_{1\text{LineEq}} = 0.1714i \text{pu}$$



$$Z_1 := \left(\frac{1}{Z_{1S}} + \frac{1}{Z_{1\text{LineEq}} + Z_{1R}} \right)^{-1}$$

$$Z_1 = 0.0689i \text{pu}$$

$$Z_2 := Z_1$$

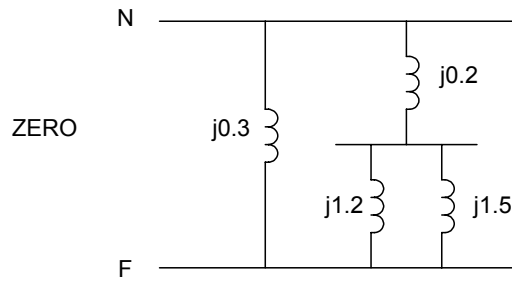

$$Z_{0S} := j \cdot 0.3 \text{ pu} \quad Z_{0R} := j \cdot 0.2 \text{ pu}$$

$$Z_{0L1} := j \cdot 1.2 \quad Z_{0L2} := j \cdot 1.5$$


$$Z_{0LineEq} := \left(\frac{1}{Z_{0L1}} + \frac{1}{Z_{0L2}} \right)^{-1}$$

$$Z_{0LineEq} = 0.6667 \text{ i pu}$$


$$Z_0 := \left(\frac{1}{Z_{0S}} + \frac{1}{Z_{0LineEq} + Z_{0R}} \right)^{-1}$$

$$Z_0 = 0.2229 \text{ i pu}$$


Solution for 4b): Three Phase Fault

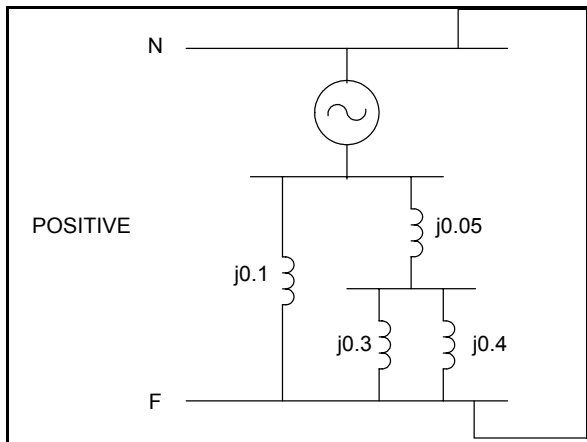


Problem 4b: Line to line fault:

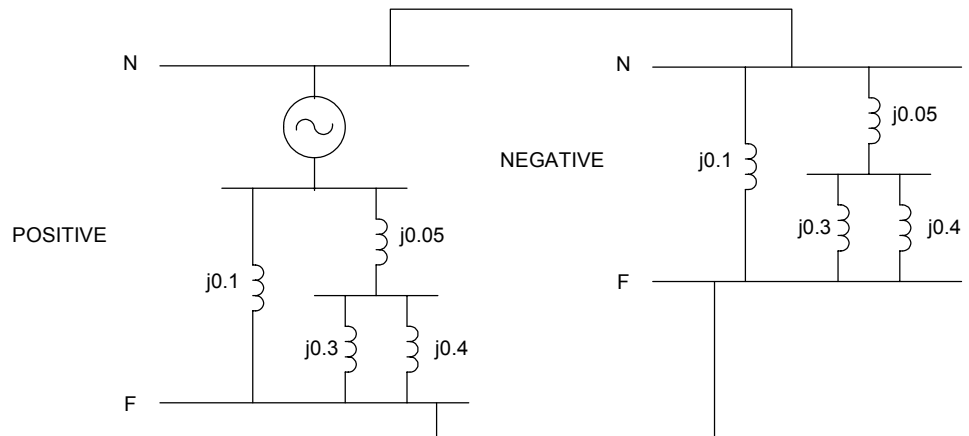

Problem 4b: Double Line to Ground Fault:

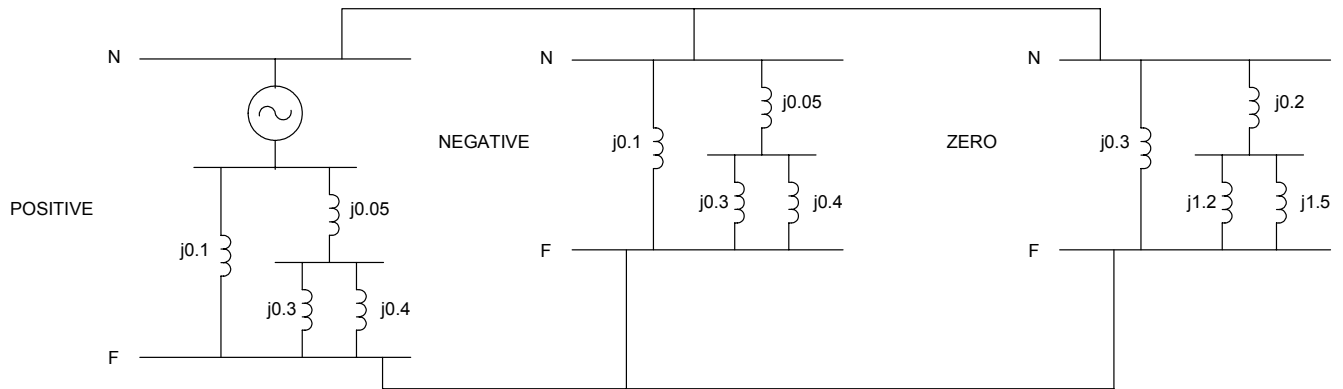

Problem 4b: Single line to ground fault:

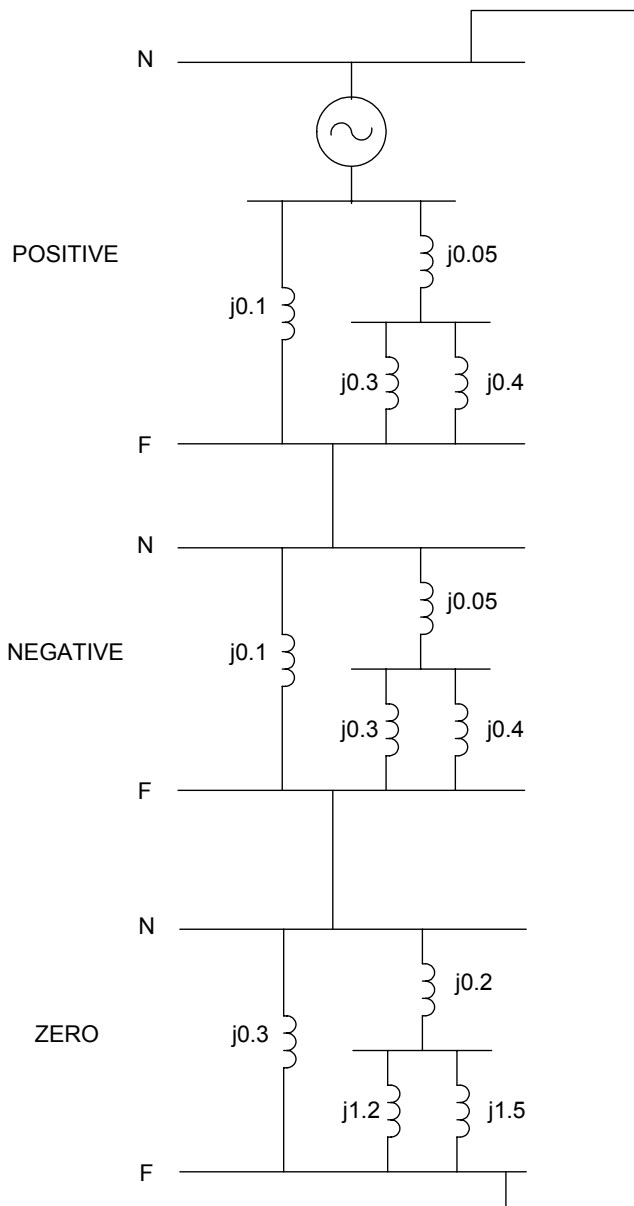

c. Determine the positive-, negative-, and zero-sequence currents and voltages at location F for a single-phase to ground fault.

Assuming the fault is on phase A:

$$I_{0F} := \frac{1.0}{Z_1 + Z_2 + Z_0} \quad |I_{0F}| = 2.7729 \text{ pu} \quad I_{1F} := I_{0F} \quad I_{2F} := I_{0F}$$


$$I_{AF} := I_{0F} + I_{1F} + I_{2F} \quad |I_{AF}| = 8.3187 \text{ pu}$$

$$V_0 := -I_{0F} \cdot Z_0 \quad |V_0| = 0.618 \text{ pu} \quad \arg(V_0) = 180 \text{ deg}$$

$$V_1 := 1.0 - I_{1F} \cdot Z_1 \quad |V_1| = 0.809 \text{ pu} \quad \arg(V_1) = 0 \text{ deg}$$

$$V_2 := -I_{2F} \cdot Z_2 \quad |V_2| = 0.191 \text{ pu} \quad \arg(V_2) = 180 \text{ deg}$$

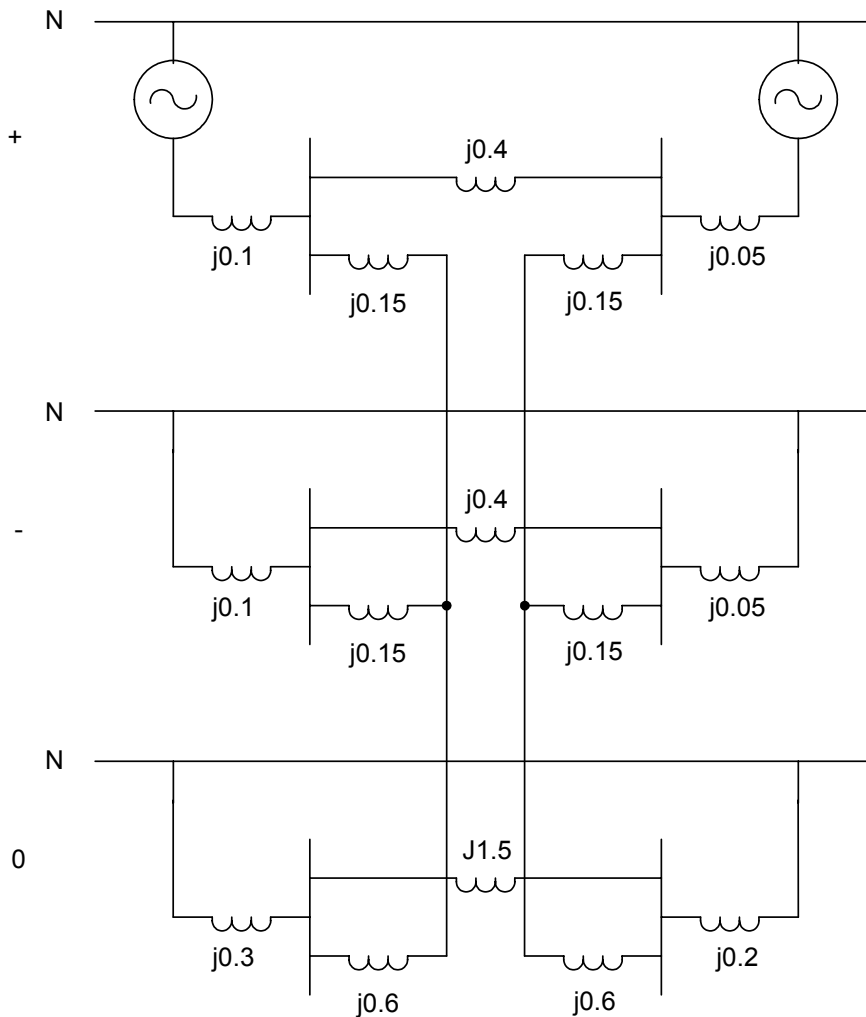5. For the system shown in 4, develop the sequence connection diagram for a single-phase open on Line 1.



$$Z_{1\text{equiv}} := \frac{Z_{1L1}}{2} + \left(\frac{1}{Z_{1S} + Z_{1R}} + \frac{1}{Z_{1L2}} \right)^{-1} + \frac{Z_{1L1}}{2} \quad Z_{1\text{equiv}} = 0.4091\text{ipu}$$

$$Z_{2\text{equiv}} := Z_{1\text{equiv}}$$

$$Z_{0\text{equiv}} := Z_{0L1} + \left(\frac{1}{Z_{0S} + Z_{0R}} + \frac{1}{Z_{0L2}} \right)^{-1} \quad Z_{0\text{equiv}} = 1.575\text{ipu}$$

6. Using the sequence diagram from problem 5, calculate the positive-, negative-, and zero-sequence currents on Line 2 with $V_R = 1 \text{ pu} @ 20 \text{ degrees}$.

$$V_S := 1 \text{ pu} \cdot e^{j \cdot 0 \text{ deg}}$$

$$V_R := 1 \text{ pu} \cdot e^{j \cdot 20 \text{ deg}}$$

Total prefault current:

$$I_{\text{sourceprefault}} := \frac{V_S - V_R}{Z_{1S} + Z_{1R} + \left(\frac{1}{Z_{1L1}} + \frac{1}{Z_{1L2}} \right)^{-1}} \quad \begin{array}{l} |I_{\text{sourceprefault}}| = 1.0805 \text{ pu} \\ \arg(I_{\text{sourceprefault}}) = -170 \text{ deg} \end{array}$$

Current dividers to find the current in lines 1 and 2:

$$I_{L1_prefault} := I_{\text{sourceprefault}} \cdot \left(\frac{Z_{1L2}}{Z_{1L1} + Z_{1L2}} \right) \quad \begin{array}{l} |I_{L1_prefault}| = 0.6174 \text{ pu} \\ \arg(I_{L1_prefault}) = -170 \text{ deg} \end{array}$$


$$I_{L2_prefault} := I_{\text{sourceprefault}} \cdot \left(\frac{Z_{1L1}}{Z_{1L1} + Z_{1L2}} \right) \quad \begin{array}{l} |I_{L2_prefault}| = 0.4631 \text{ pu} \\ \arg(I_{L2_prefault}) = -170 \text{ deg} \end{array}$$

$$I_{\text{ABCL1_prefault}} := I_{L1_prefault} \cdot \begin{pmatrix} 1 \\ a^2 \\ a \end{pmatrix} \quad \begin{array}{l} \overrightarrow{|I_{\text{ABCL1_prefault}}|} = \begin{pmatrix} 0.6174 \\ 0.6174 \\ 0.6174 \end{pmatrix} \text{ pu} \\ \overrightarrow{\arg(I_{\text{ABCL1_prefault}})} = \begin{pmatrix} -170 \\ 70 \\ -50 \end{pmatrix} \text{ deg} \end{array}$$

$$I_{\text{ABCL2_prefault}} := I_{L2_prefault} \cdot \begin{pmatrix} 1 \\ a^2 \\ a \end{pmatrix} \quad \overrightarrow{|I_{\text{ABCL2_prefault}}|} = \begin{pmatrix} 0.4631 \\ 0.4631 \\ 0.4631 \end{pmatrix} \text{ pu}$$

$$\overrightarrow{\arg(I_{ABCL2_prefault})} = \begin{pmatrix} -170 \\ 70 \\ -50 \end{pmatrix} \text{ deg}$$

Phase A open analysis:

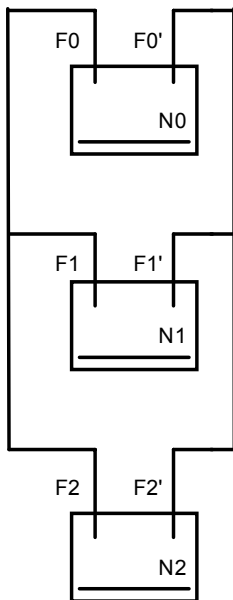

Equivalent voltage source for phase A open analysis:

$$V_{se} := V_S - V_R \quad V_{se} = 0.0603 - 0.342i \text{ pu}$$

Norton Equivalent Current:
$$I_{se} := \frac{V_{se}}{Z_{1R} + Z_{1S}}$$

$$I_{se} = -2.2801 - 0.402i \text{ pu}$$

Equivalent Parallel Impedance:
$$Z_{eq} := \left(\frac{1}{Z_{1L2}} + \frac{1}{Z_{1S} + Z_{1R}} \right)^{-1}$$

$$Z_{eq} = 0.1091i \text{ pu}$$

Convert back to Thevenin Equivalent Voltage

$$V_f := Z_{eq} \cdot I_{se} \quad |V_f| = 0.2526 \text{ pu} \quad \arg(V_f) = -80 \text{ deg}$$

Positive sequence current in line 1:

$$I_{1L1_open} := \frac{V_f}{Z_{1equiv} + \left(\frac{1}{Z_{2equiv}} + \frac{1}{Z_{0equiv}} \right)^{-1}} \quad |I_{1L1_open}| = 0.3442 \text{ pu}$$

$$\arg(I_{1L1_open}) = -170 \text{ deg}$$

Negative sequence current in line 1 (current divider on the line 1 current)

$$I_{2L1_open} := -I_{1L1_open} \cdot \frac{Z_{0equiv}}{Z_{2equiv} + Z_{0equiv}} \quad |I_{2L1_open}| = 0.2732 \text{ pu}$$

$$\arg(I_{2L1_open}) = 10 \text{ deg}$$

Zero sequence current in line 1 (current divider on the line 1 current)

$$I_{0L1_open} := -I_{1L1_open} \cdot \frac{Z_{2equiv}}{Z_{2equiv} + Z_{0equiv}} \quad |I_{0L1_open}| = 0.071 \text{ pu}$$

$$\arg(I_{0L1_open}) = 10 \text{ deg}$$

$$I_{ABC_Line1} := A_{012} \cdot \begin{pmatrix} I_{0L1_open} \\ I_{1L1_open} \\ I_{2L1_open} \end{pmatrix} \quad \overrightarrow{|I_{ABC_Line1}|} = \begin{pmatrix} 0 \\ 0.5452 \\ 0.5452 \end{pmatrix} \text{ pu}$$

$$\arg(I_{ABC_Line1_2}) = 88.7404 \text{ deg}$$

$$\arg(I_{ABC_Line1_3}) = -68.7404 \text{ deg}$$

Note that the magnitude on phase A is 0 and a little smaller on the unfaulted phases. There is also a phase shift compared to pre-fault

Now to find the line 2 current, we need to do another current divider on each of the sequence currents from line 1, since the sequence currents could either pass through the sources or line 1 to return to line 1.

Positive sequence load current in line two ignoring open line

$$I_{LineA2} := \frac{V_S - V_R}{Z_{1S} + Z_{1L2} + Z_{1R}} \quad |I_{LineA2}| = 0.631$$

$$\arg(I_{LineA2}) = -170 \text{ deg}$$

$$I_{1L2} := -I_{1L1_open} \cdot \left(\frac{Z_{1S} + Z_{1R}}{Z_{1S} + Z_{1R} + Z_{1L2}} \right) + I_{LineA2} \quad |I_{1L2}| = 0.5376 \text{ pu} \quad \arg(I_{1L2}) = -170 \text{ deg}$$

$$I_{2L2} := -I_{2L1_open} \cdot \left(\frac{Z_{1S} + Z_{1R}}{Z_{1S} + Z_{1R} + Z_{1L2}} \right) \quad |I_{2L2}| = 0.0745 \text{ pu} \quad \arg(I_{2L2}) = -170 \text{ deg}$$

$$I_{0L2} := -I_{0L1_open} \cdot \left(\frac{Z_{0S} + Z_{0R}}{Z_{0S} + Z_{0R} + Z_{0L2}} \right) \quad |I_{0L2}| = 0.0177 \text{ pu} \quad \arg(I_{0L2}) = -170 \text{ deg}$$

$$I_{ABC_Line2} := A_{012} \cdot \begin{pmatrix} I_{0L2} \\ I_{1L2} \\ I_{2L2} \end{pmatrix} \quad \overrightarrow{|I_{ABC_Line2}|} = \begin{pmatrix} 0.6298 \\ 0.4939 \\ 0.4939 \end{pmatrix} \text{ pu} \quad \arg(I_{ABC_Line2}) = \begin{pmatrix} -170 \\ 64.2868 \\ -44.2868 \end{pmatrix} \text{ deg}$$