
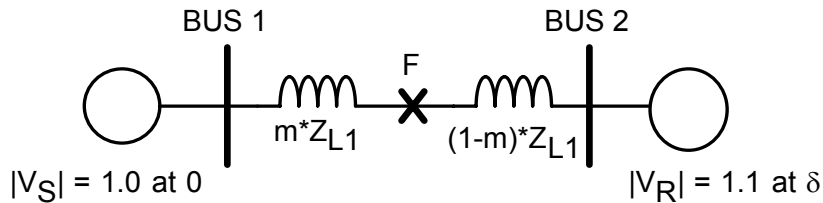


Fault Calculations with Power Flow

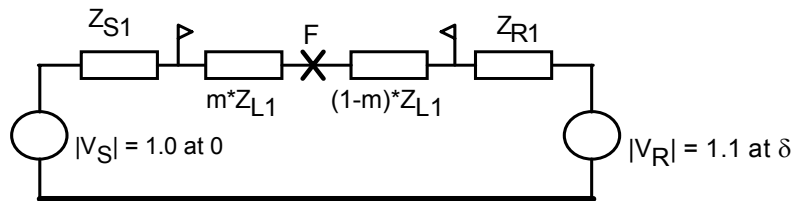- The system below has a pre-fault power flow condition due to the angle and magnitude differences between the sources.
- The fault calculations need to change a little to ensure that the positive sequence current reflects this power flow in the case of a fault where power flow can continue to flow.
- Lets look at a SLG fault case.



- The negative and zero sequence circuits will be the same as one would in a case where the sources have equal angles and magnitudes, so they will not be described here.
- Positive sequence equivalent circuit:



- There are effectively two components to the current seen at each relay, and they can be determined using superposition.
 1. The fault current that flows due to the fault and leave this network at point F and reenters from the neutral plane.
 2. The current that flows between the two sources, the load current.

1. Determining fault current


- We need to find a Thevenin equivalent circuit.
- The process is actually a standard circuit analysis approach (Millman's Theorem), but is typically avoided if the voltage sources are all assumed to have the same magnitude and angle.
 1. Convert the two sources to their Norton equivalents, using the impedance between the source and the fault point. Note that these are phasor calculations.

$$Z_{\text{left1}} = Z_{S1} + m \cdot Z_{L1}$$

$$Z_{\text{right1}} = Z_{R1} + (1 - m) \cdot Z_{L1}$$

$$I_{\text{Norton_left}} = \frac{V_{S1}}{Z_{\text{left1}}}$$

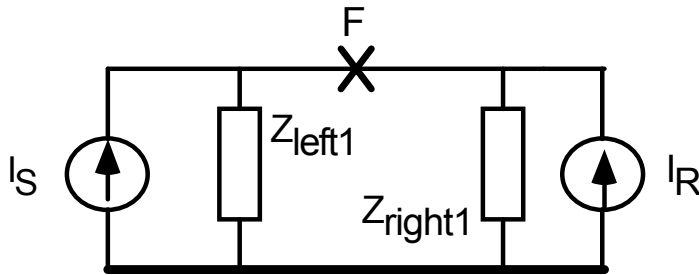
$$I_{\text{Norton_right}} = \frac{V_{R1}}{Z_{\text{right1}}}$$



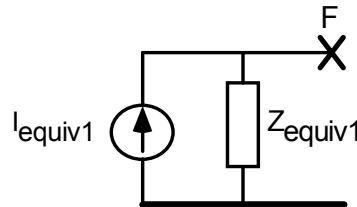2. Note that the impedances are in parallel and the current sources are effectively in parallel
- Combine the impedances in parallel
 - Combine the two current sources (note that this is not limited to two sources)

$$Z_{equiv1} = \left(\frac{1}{Z_{left1}} + \frac{1}{Z_{right1}} \right)^{-1}$$


$$I_{equiv1} = I_{Norton_left} + I_{Norton_right}$$



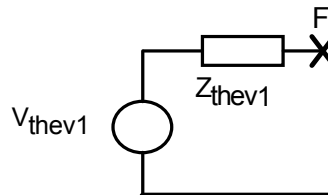- c. Then convert back to a Thevenin equivalent

$$Z_{thev1} = Z_{equiv1}$$

$$V_{thev1} = I_{equiv1} \cdot Z_{equiv1}$$



- This Thevenin equivalent source is used for the fault calculations. ***But not for the power flow calculation***
 - Note that the Thevenin impedance is the same as we always do.
 - Now the voltage source has a magnitude and angle that reflects the difference between the two sources.
 - If the sources both have the same magnitude and angle, the resulting Thevenin voltage source will match that.

2. Determining power flow current

- This is just like any other power flow calculation. In this case you can look between the two known source voltages and the **total impedance** between them. In other cases you might need to find V1 and V2 and just use the line impedance.

$$I_{12} = \frac{V_{S1} - V_{R1}}{Z_{S1} + Z_{L1} + Z_{R1}}$$

$$I_{21} = \frac{V_{R1} - V_{S1}}{(Z_{S1} + Z_{L1} + Z_{R1})}$$

- Notes:
 1. The fault location doesn't matter in this calculation
 2. The Thevenin equivalent source from above is not used
 3. I_{12} flows in the opposite direction I_{21}

3. Total sequence currents

- The positive sequence current for the relay at bus 1 (phasor sums):

$$I_{\text{Relay1}} = I_{f_relay1} + I_{12_relay1}$$

$$I_{\text{Relay2}} = I_{f_relay2} - I_{12_relay1}$$

- I_{f_relay1} and I_{f_relay2} come from current dividers as usual
- The negative and zero sequence currents do not include an load flow current and are simply from current dividers from the fault calculation.

Example

pu := 1 MVA := 1000kW S_{base} := 100MVA kV_{base} := 500kV

$$a := 1 \cdot e^{j \cdot 120 \text{deg}} \quad A_{012} := \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix}$$

- System parameters

$$\begin{aligned} Z_{sL1} &:= (0.0006 + j \cdot 0.02079) \text{pu} & Z_{rL1} &:= (0.00067 + j \cdot 0.01633) \text{pu} & Z_{rL2} &:= Z_{rL1} \\ Z_{sL0} &:= (0.0021 + j \cdot 0.02037) \text{pu} & Z_{rL0} &:= (0.00065 + j \cdot 0.01429) \text{pu} & & \\ Z_{sL2} &:= Z_{sL1} & Z_{L1} &:= (0.00205 + j \cdot 0.02893) \text{pu} & Z_{L2} &:= Z_{L1} \\ & & Z_{L0} &:= (0.01708 + j \cdot 0.10764) \text{pu} & & \end{aligned}$$


$$Z_{\text{base}} := \frac{\text{kV}_{\text{base}}^2}{S_{\text{base}}} \quad Z_{\text{base}} = 2500 \Omega$$

$$V_{S1} := \left(\frac{500 \text{kV}}{\text{kV}_{\text{base}}} \right) e^{j \cdot 0 \text{deg}} \quad V_{R1} := \left(\frac{500 \text{kV}}{\text{kV}_{\text{base}}} \right) e^{-j \cdot 30 \text{deg}}$$

- Now we need to find the Thevenin equivalent with the unbalanced sources included.

Fault location: M := 0.3


Sequence equivalent circuits:

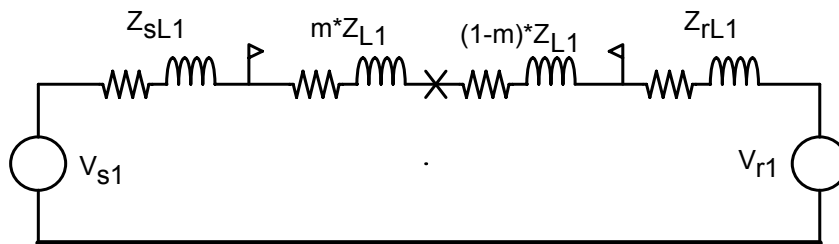


M := 0.3

$$Z_{\text{thev1}} := \left[\frac{1}{Z_{sL1} + M \cdot Z_{L1}} + \frac{1}{Z_{rL1} + (1 - M) \cdot Z_{L1}} \right]^{-1}$$

$$|Z_{\text{thev1}}| = 0.0163 \quad \arg(Z_{\text{thev1}}) = 87.2232 \text{ deg}$$

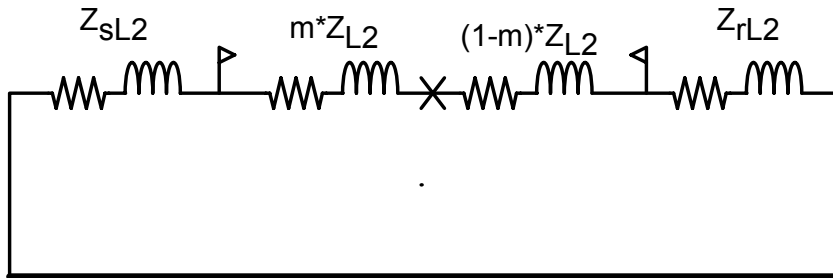

$$Z_{\text{thev2}} := Z_{\text{thev1}}$$

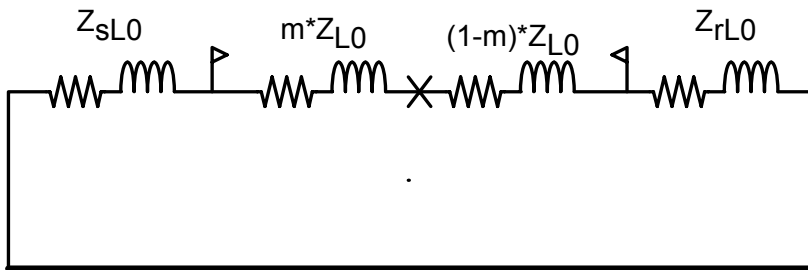

$$Z_{\text{thev0}} := \left[\frac{1}{Z_{sL0} + M \cdot Z_{L0}} + \frac{1}{Z_{rL0} + (1 - M) \cdot Z_{L0}} \right]^{-1}$$

$$|Z_{\text{thev0}}| = 0.0335 \quad \arg(Z_{\text{thev0}}) = 82.1172 \text{ deg}$$

$$I_{s1\text{Nor}} := \frac{V_{S1}}{Z_{sL1} + M \cdot Z_{L1}}$$

$$I_{r1\text{Nor}} := \frac{V_{R1}}{Z_{rL1} + (1 - M) \cdot Z_{L1}}$$

$$I_{1_Nor} := I_{s1\text{Nor}} + I_{r1\text{Nor}}$$

$$V_{1_Thev} := I_{1_Nor} \cdot Z_{\text{thev1}} \quad |V_{1_Thev}| = 0.9684 \text{ pu} \quad \arg(V_{1_Thev}) = -13.3447 \text{ deg}$$

$$I_{f0}(R_f) := \frac{V_{1_Thev}}{Z_{\text{thev0}} + Z_{\text{thev1}} + Z_{\text{thev2}} + 3 \cdot R_f}$$

$$I_{f1}(R_f) := I_{f0}(R_f)$$


$$I_{f2}(R_f) := I_{f0}(R_f)$$

- Voltages and Currents at Relay A:

$$I_{fA1}(R_f) := I_{f1}(R_f) \cdot \left[\frac{Z_{rL1} + (1 - M) \cdot Z_{L1}}{(Z_{sL1} + M \cdot Z_{L1}) + [Z_{rL1} + (1 - M) \cdot Z_{L1}]} \right]$$

$$|I_{fA1}(0pu)| = 8.1165 \quad \arg(I_{fA1}(0pu)) = -98.3996 \text{ deg}$$

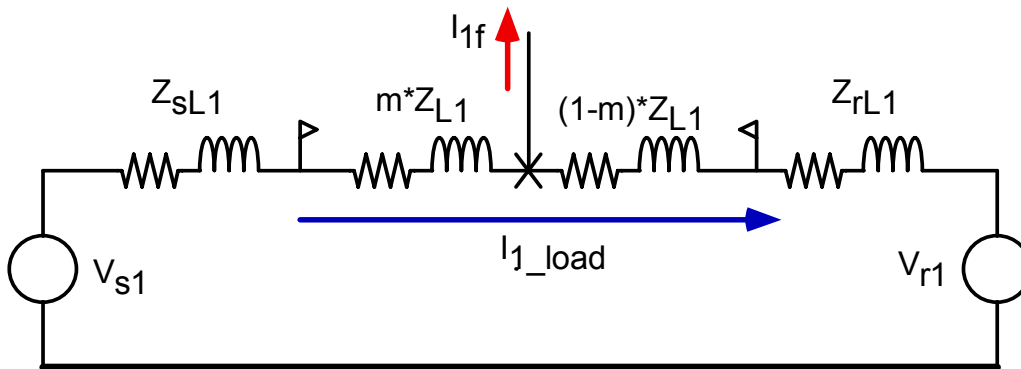However, the positive sequence current seen by the relay will include the load current



$$I_{1_load} := \frac{V_{S1} - V_{R1}}{Z_{sL1} + Z_{L1} + Z_{rL1}} \quad \arg(V_{R1}) = -30 \text{ deg}$$

$$|I_{1_load}| = 7.8272 \quad \arg(I_{1_load}) = -12.1225 \text{ deg} \quad I_{base} := \frac{S_{base}}{\sqrt{3} \cdot kV_{base}}$$

$$|I_{1_load}| \cdot I_{base} = 903.8052 \text{ A}$$

$$I_{relayA1}(R_f) := I_{fA1}(R_f) + I_{1_load}$$

$$I_{relayA1}(0pu) = 6.467 - 9.6732i \quad |I_{relayA1}(0pu)| = 11.6358$$

$$\arg(I_{relayA1}(0pu)) = -56.2352 \text{ deg}$$

$$|I_{relayA1}(0pu)| \cdot I_{base} = 1.3436 \times 10^3 \text{ A}$$

$$I_{relayA2}(R_f) := I_{f2}(R_f) \cdot \left[\frac{Z_{rL2} + (1 - M) \cdot Z_{L2}}{(Z_{sL2} + M \cdot Z_{L2}) + [Z_{rL2} + (1 - M) \cdot Z_{L2}]} \right]$$

$$|I_{relayA2}(0pu)| = 8.1165 \quad \arg(I_{relayA2}(0pu)) = -98.3996 \text{ deg}$$

No negative or zero sequence load flow

$$I_{\text{relayA0}}(R_f) := I_{f0}(R_f) \cdot \left[\frac{Z_{fL0} + (1 - M) \cdot Z_{L0}}{(Z_{sL0} + M \cdot Z_{L0}) + [Z_{fL0} + (1 - M) \cdot Z_{L0}]} \right]$$

$$|I_{\text{relayA0}}(0\text{pu})| = 9.2295 \quad \arg(I_{\text{relayA0}}(0\text{pu})) = -98.0557 \text{ deg}$$

$$V_{\text{relayA1}}(R_f) := V_{S1} - I_{\text{relayA1}}(R_f) \cdot (Z_{sL1})$$

$$|V_{\text{relayA1}}(0\text{pu})| = 0.8054 \text{ pu}$$

$$\arg(V_{\text{relayA1}}(0\text{pu})) = -9.1916 \text{ deg}$$

$$V_{\text{relayA2}}(R_f) := -I_{\text{relayA2}}(R_f) \cdot (Z_{sL2})$$

$$|V_{\text{relayA2}}(0\text{pu})| = 0.1688 \text{ pu}$$

$$\arg(V_{\text{relayA2}}(0\text{pu})) = 169.9473 \text{ deg}$$

$$V_{\text{relayA0}}(R_f) := -I_{\text{relayA0}}(R_f) \cdot (Z_{sL0})$$

$$|V_{\text{relayA0}}(0\text{pu})| = 0.189 \text{ pu}$$

$$\arg(V_{\text{relayA0}}(0\text{pu})) = 166.0583 \text{ deg}$$

$$I_{\text{ABC_RA}}(R_f) := A_{012} \cdot \begin{pmatrix} I_{\text{relayA0}}(R_f) \\ I_{\text{relayA1}}(R_f) \\ I_{\text{relayA2}}(R_f) \end{pmatrix}$$

$$V_{\text{ABC_RA}}(R_f) := A_{012} \cdot \begin{pmatrix} V_{\text{relayA0}}(R_f) \\ V_{\text{relayA1}}(R_f) \\ V_{\text{relayA2}}(R_f) \end{pmatrix}$$

$$\overrightarrow{|I_{\text{ABC_RA}}(0\text{pu})|} = \begin{pmatrix} 27.1357 \\ 8.7473 \\ 6.8192 \end{pmatrix} \text{ pu}$$

$$\overrightarrow{\arg(I_{\text{ABC_RA}}(0\text{pu}))} = \begin{pmatrix} -81.5489 \\ -127.7695 \\ 111.6023 \end{pmatrix} \text{ deg}$$

$$\overrightarrow{|V_{\text{ABC_RA}}(0\text{pu})|} = \begin{pmatrix} 0.4486 \\ 0.9729 \\ 0.9953 \end{pmatrix} \text{ pu}$$

$$\overrightarrow{\arg(V_{\text{ABC_RA}}(0\text{pu}))} = \begin{pmatrix} -6.8679 \\ -130.7249 \\ 111.26 \end{pmatrix} \text{ deg}$$

$$\overrightarrow{|I_{\text{ABC_RA}}(0\text{pu})|} \cdot I_{\text{base}} = \begin{pmatrix} 3133.359 \\ 1010.047 \\ 787.413 \end{pmatrix} \text{ A}$$

$$\overrightarrow{|V_{\text{ABC_RA}}(0\text{pu})|} \cdot \frac{\text{kV}_{\text{base}}}{\sqrt{3}} = \begin{pmatrix} 129.4936 \\ 280.8579 \\ 287.3233 \end{pmatrix} \text{ kV}$$

- Voltages and Currents at Relay B:

$$I_{fB1}(R_f) := I_{f1}(R_f) \cdot \left[\frac{Z_{sL1} + M \cdot Z_{L1}}{(Z_{sL1} + M \cdot Z_{L1}) + [Z_{rL1} + (1 - M) \cdot Z_{L1}]} \right]$$

$$|I_{fB1}(0pu)| = 6.5333 \quad \arg(I_{fB1}(0pu)) = -97.4672 \text{ deg}$$

Again, we need to incorporate load flow. In this case it will be subtracted from the relay current due to the polarity of the load current compared to the fault current

$$I_{\text{relayB1}}(R_f) := I_{fB1}(R_f) - I_{1_load} \quad |I_{\text{relayB1}}(0pu)| = 9.78 \text{ pu}$$

$$\arg(I_{\text{relayB1}}(0pu)) = -150.3772 \text{ deg}$$

$$I_{\text{relayB2}}(R_f) := I_{f2}(R_f) \cdot \left[\frac{Z_{sL2} + M \cdot Z_{L2}}{(Z_{sL2} + M \cdot Z_{L2}) + [Z_{rL2} + (1 - M) \cdot Z_{L2}]} \right]$$

$$|I_{\text{relayB2}}(0pu)| = 6.5333 \quad \arg(I_{\text{relayB2}}(0pu)) = -97.4672 \text{ deg}$$

$$I_{\text{relayB0}}(R_f) := I_{f0}(R_f) \cdot \left[\frac{Z_{sL0} + M \cdot Z_{L0}}{(Z_{sL0} + M \cdot Z_{L0}) + [Z_{rL0} + (1 - M) \cdot Z_{L0}]} \right]$$

$$|I_{\text{relayB0}}(0pu)| = 5.4198 \quad \arg(I_{\text{relayB0}}(0pu)) = -97.8614 \text{ deg}$$

$$V_{\text{relayB1}}(R_f) := V_{R1} - I_{\text{relayB1}}(R_f) \cdot (Z_{rL1}) \quad |V_{\text{relayB1}}(0pu)| = 0.8698 \text{ pu}$$

$$\arg(V_{\text{relayB1}}(0pu)) = -24.2985 \text{ deg}$$

$$V_{\text{relayB2}}(R_f) := -I_{\text{relayB2}}(R_f) \cdot (Z_{rL2}) \quad |V_{\text{relayB2}}(0pu)| = 0.1068 \text{ pu}$$

$$\arg(V_{\text{relayB2}}(0pu)) = 170.1833 \text{ deg}$$

$$V_{\text{relayB0}}(R_f) := -I_{\text{relayB0}}(R_f) \cdot (Z_{rL0}) \quad |V_{\text{relayB0}}(0pu)| = 0.0775 \text{ pu}$$

$$\arg(V_{\text{relayB0}}(0pu)) = 169.5342 \text{ deg}$$

$$I_{ABC_RB}(R_f) := A_{012} \cdot \begin{pmatrix} I_{\text{relayB0}}(R_f) \\ I_{\text{relayB1}}(R_f) \\ I_{\text{relayB2}}(R_f) \end{pmatrix} \quad V_{ABC_RB}(R_f) := A_{012} \cdot \begin{pmatrix} V_{\text{relayB0}}(R_f) \\ V_{\text{relayB1}}(R_f) \\ V_{\text{relayB2}}(R_f) \end{pmatrix}$$

$$\overrightarrow{|I_{ABC_RB}(0\text{pu})|} = \begin{pmatrix} 19.4961 \\ 8.7473 \\ 6.8192 \end{pmatrix} \text{ pu}$$


$$\overrightarrow{\arg(I_{ABC_RB}(0\text{pu}))} = \begin{pmatrix} -121.1744 \\ 52.2305 \\ -68.3977 \end{pmatrix} \text{ deg}$$

$$\overrightarrow{|V_{ABC_RB}(0\text{pu})|} = \begin{pmatrix} 0.6926 \\ 0.9533 \\ 0.9662 \end{pmatrix} \text{ pu}$$

$$\overrightarrow{\arg(V_{ABC_RB}(0\text{pu}))} = \begin{pmatrix} -28.0432 \\ -141.4748 \\ 95.5995 \end{pmatrix} \text{ deg}$$

$$\overrightarrow{|I_{ABC_RB}(0\text{pu})|} \cdot I_{\text{base}} = \begin{pmatrix} 2251.22 \\ 1010.05 \\ 787.41 \end{pmatrix} \text{ A}$$

$$\overrightarrow{|V_{ABC_RB}(0\text{pu})|} \cdot \frac{\text{kV}_{\text{base}}}{\sqrt{3}} = \begin{pmatrix} 199.9506 \\ 275.1805 \\ 278.9299 \end{pmatrix} \text{ kV}$$

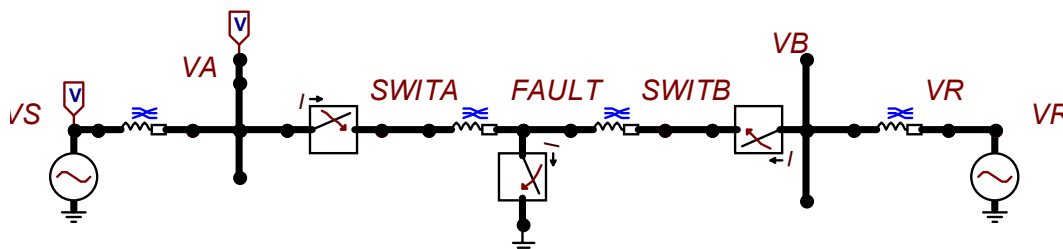

$$V_{A_A} := 129.7\text{kV} \quad \text{at} \quad -6.2\text{deg}$$

$$V_{A_B} := 280.8\text{kV} \quad \text{at} \quad -130.1\text{deg}$$

$$V_{A_C} := 286.9\text{kV} \quad \text{at} \quad 112.0\text{deg}$$

$$I_{A_A} := 3127\text{A} \quad \text{at} \quad -80.8\text{deg}$$

$$I_{B_A} := 2249\text{A} \quad \text{at} \quad -120.6\text{deg}$$

$$I_{A_B} := 1009\text{A} \quad \text{at} \quad -127.2\text{deg}$$

$$I_{B_B} := 1009\text{A} \quad \text{at} \quad 52.84\text{deg}$$

$$I_{A_C} := 786.2\text{kV} \quad \text{at} \quad 112.4\text{deg}$$

$$I_{B_C} := 786.2\text{kV} \quad \text{at} \quad -67.6\text{deg}$$